

Lecture 5: DC & Transient Response

Outline


- ☐ Pass Transistors
- ☐ DC Response
- ☐ Logic Levels and Noise Margins
- ☐ Transient Response
- ☐ RC Delay Models
- ☐ Delay Estimation

Transistor Operation

- ❑ Current depends on region of transistor behavior
- ❑ For what V_{in} and V_{out} are nMOS and pMOS in
 - Cutoff?
 - Linear?
 - Saturation?

nMOS Operation

Cutoff	Linear	Saturated
$V_{gsn} <$	$V_{gsn} >$	$V_{gsn} >$
	$V_{dsn} <$	$V_{dsn} >$

 


pMOS Operation

Cutoff	Linear	Saturated
$V_{gsp} > V_{tp}$ $V_{in} > V_{DD} + V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{DD} + V_{tp}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$

$$V_{gsp} = V_{in} - V_{DD}$$


$$V_{tp} < 0$$

$$V_{dsp} = V_{out} - V_{DD}$$

 


I-V Characteristics

 - Make pMOS is wider than nMOS such that $\beta_n = \beta_p$




Current vs. V_{out} , V_{in}

 


Load Line Analysis

- For a given V_{in} :
 - Plot I_{dsn} , I_{dsp} vs. V_{out}
 - V_{out} must be where |currents| are equal in


 


Load Line Analysis

 


DC Transfer Curve

  □ Transcribe points onto V_{in} vs. V_{out} plot




Operating Regions

- Revisit transistor operating regions

 


Region	nMOS	pMOS
A		
B		
C		
D		
E		

 

Beta Ratio

 - ❑ If $\beta_p / \beta_n \neq 1$, switching point will move from $V_{DD}/2$
- ❑ Called *skewed* gate
- ❑ Other gates: collapse into equivalent inverter



Layout Comparison

❑ Which layout is better?

